
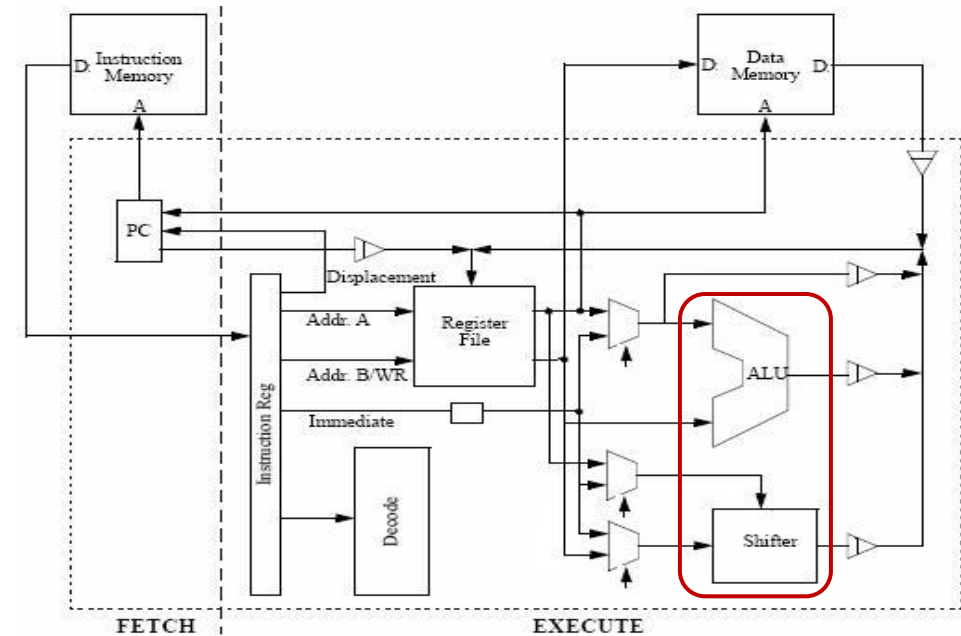


# Lab 2: Design Execution Part

~~10/3 — 10/11 (11:59:59 pm)~~

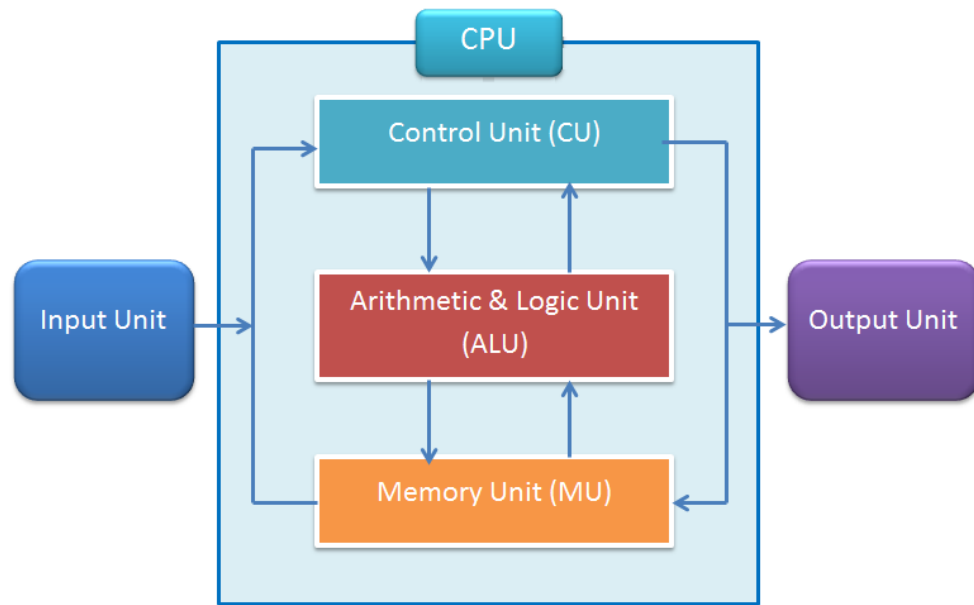
# Execution Part

- Use ALU or shifter to perform operations on data
- Might output execution flags used for branch/jump



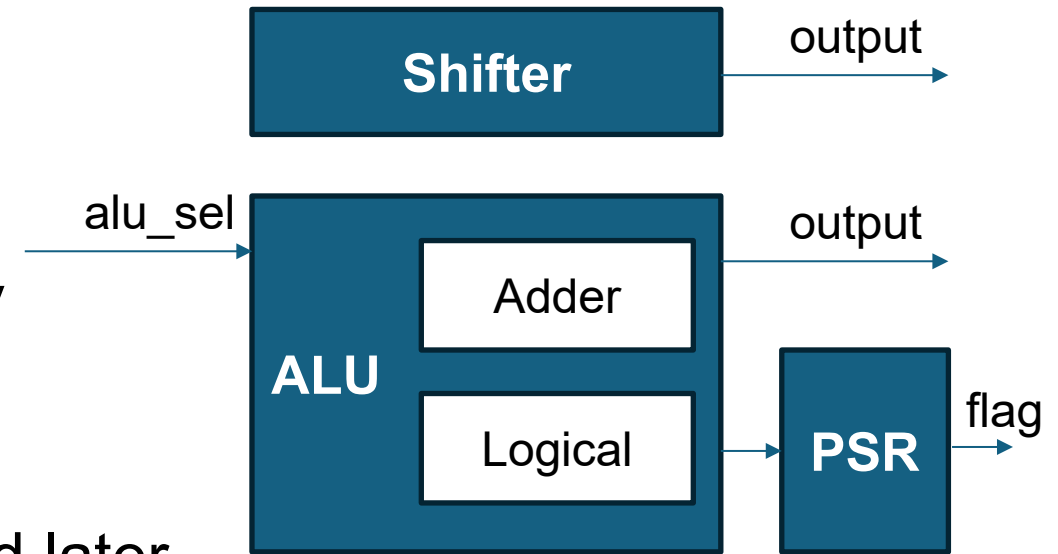
# Execution Consists of...

- ALU includes followings
  - Adder: for ADD, SUB, CMP
  - Logical operators: AND/OR/XOR
  - ALU modes are defined in ALU\_ops.v
- Next to ALU...
  - Simple bidirectional shifter
  - PSR: status register of ALU, explained later
- We implement and integrate components



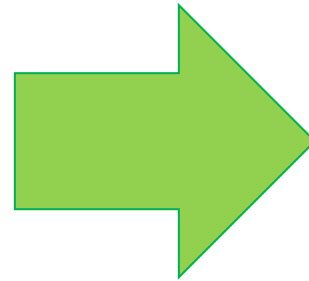
# ALU's Operation Modes in `ALU_ops.v`

- `alu_sel : 6'b100000`
  - `ADD`
- `alu_sel : 6'b010000`
  - `SUB`
- `alu_sel : 6'b001000`
  - `CMP`



 **Result as CLA's output**

- `alu_sel : 6'b000100`
  - `AND`
- `alu_sel : 6'b000010`
  - `OR`
- `alu_sel : 6'b000001`
  - `XOR`



**Result as logic's output**

# Adder: Carry Lookahead Adder (CLA)

- Assume: adder for  $A_n \dots A_0$  and  $B_n \dots B_0$
- Able to get result only using input and input carry in without knowing carryout at each bit position
- Defined new signals “propagate” and “generate”

$$p_i = A_i + B_i$$

$$g_i = A_i \cdot B_i$$

- Reform carry-out at each bit position

$$c_{i+1} = A_i \cdot B_i + A_i \cdot c_i + B_i \cdot c_i \Rightarrow c_{i+1} = g_i + p_i \cdot c_i$$

# A 4b CLA

$$c_1 = g_0 + p_0 \cdot c_0$$

$$c_2 = g_1 + p_1 \cdot c_1$$

$$= g_1 + p_1 \cdot (g_0 + p_0 \cdot c_0)$$

$$= g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0$$

$$c_3 = g_2 + p_2 \cdot c_2$$


$$= g_2 + p_2 \cdot (g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0)$$

$$= g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot c_0$$

$$c_4 = g_3 + p_3 \cdot c_3$$

$$= g_3 + p_3 \cdot (g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot c_0)$$
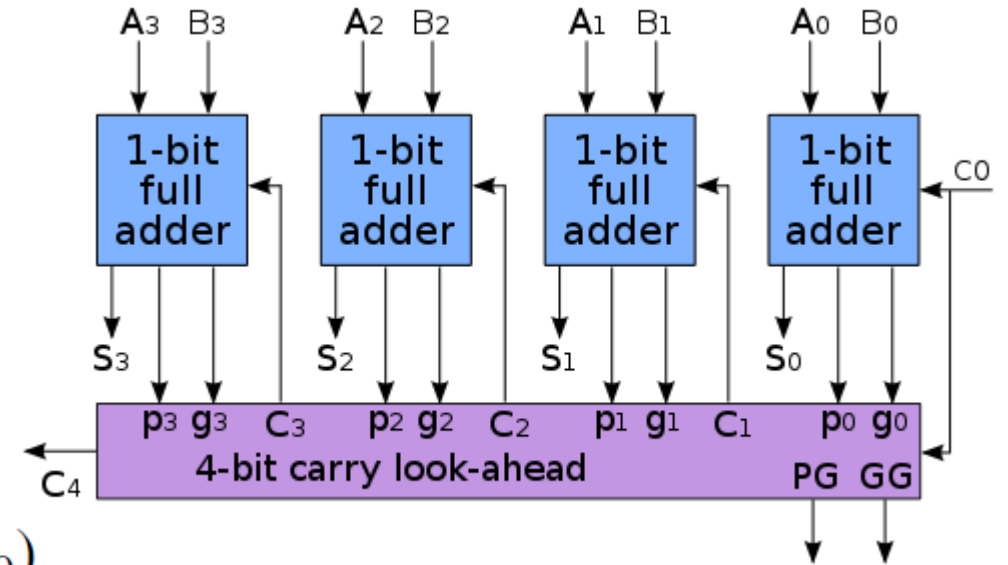
$$= g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0 + p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot c_0$$



# Extending 4b CLA as 16b Group CLA

- Components
  - Four groups of 4b CLAs
  - One lookahead carry unit (LCU)
- LCU generates carry-in to each group
- Notes
  - Provided code is slightly different from figure
  - CLA does not know input is signed or unsigned

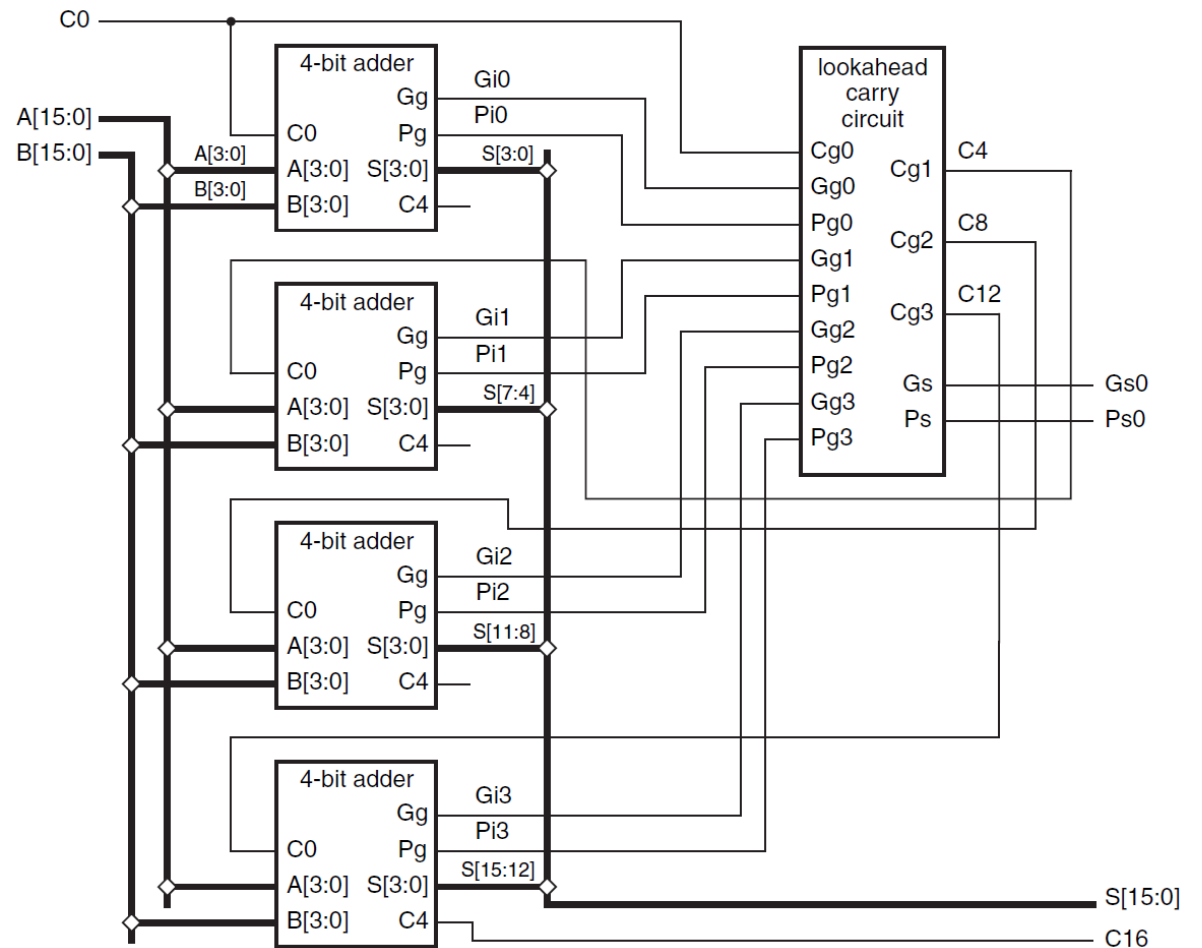


Figure 8-8 A 16-bit group-carry-lookahead adder with 4-bit groups.

# Signals of 16b CLAI in Our Code

- Input
  - A\_i: first 16b operand
  - B\_i: second 16b operand
  - CARRYIN\_i: Used to select operation mode.
    - 0:  $A_i + B_i$
    - 1:  $B_i - A_i$
- Output
  - sum\_o: calculation result of CLA in 16b
  - **flag\_overflow\_o**: overflow flags. One flag will be used at a time by the *instruction decoder* depending on the operation mode (or *opcode*)
    - [0] (C-flag): overflow that is meaningful for unsigned operations
    - [1] (F-flag): overflow that is meaningful for signed operations (2s complement)




# TODO: Implement Overflow Flags

- Case studies for understanding (0x: Hexadecimal)

A [unsigned] [signed]	B [unsigned] [signed]	CLA16b.ADD (carryout, 16b)	CLA16b.SUB (carryout, 16b)	Unsigned		Signed		F		C	
				True.ADD	True.SUB	True.ADD	True.SUB	ADD	SUB	ADD	SUB
0xDEAD [57005] [-8531]	0xCAFE [51966] [-13570]	1, 0xA9AB	0, 0xEC51	0x1_A9AB (>65535)	-5039 (not unsigned!)	0xA9AB	0xEC51	0	0	1	1
0x10AF [4271] [4271]	0xBEEF [48879] [-16657]	0, 0xCF9E	1, 0xAE40	0xCF9E	0xAE40	0xCF9E	0xAE40	0	0	0	0
0xBAAD [47789] [-17747]	0xC0DE [49374] [-16162]	1, 0x7B8B	1, 0x0631	0x1_7B8B (>65535)	0x0631	-33909 (0x7B8B>0)	0x0631	1	0	1	0
0x0003	0x0004	0, 0x0007	1, 0x0001	0x0007	0x0001	0x0007	0x0001	0	0	0	0
0x4B1D [19229] [19229]	0x10AF [4271] [4271]	0, 0x5BCC	0, 0xC592	0x5BCC	-14958 (not unsigned!)	0x5BCC	0xC592	0	0	0	1
0x5440 [21568] [21568]	0xABBA [43962] [-21574]	0, 0xFFFFA	1, 0x577A	0xFFFFA	0x577A	0xFFFFA	-43142 (0x577A>0)	0	1	0	0
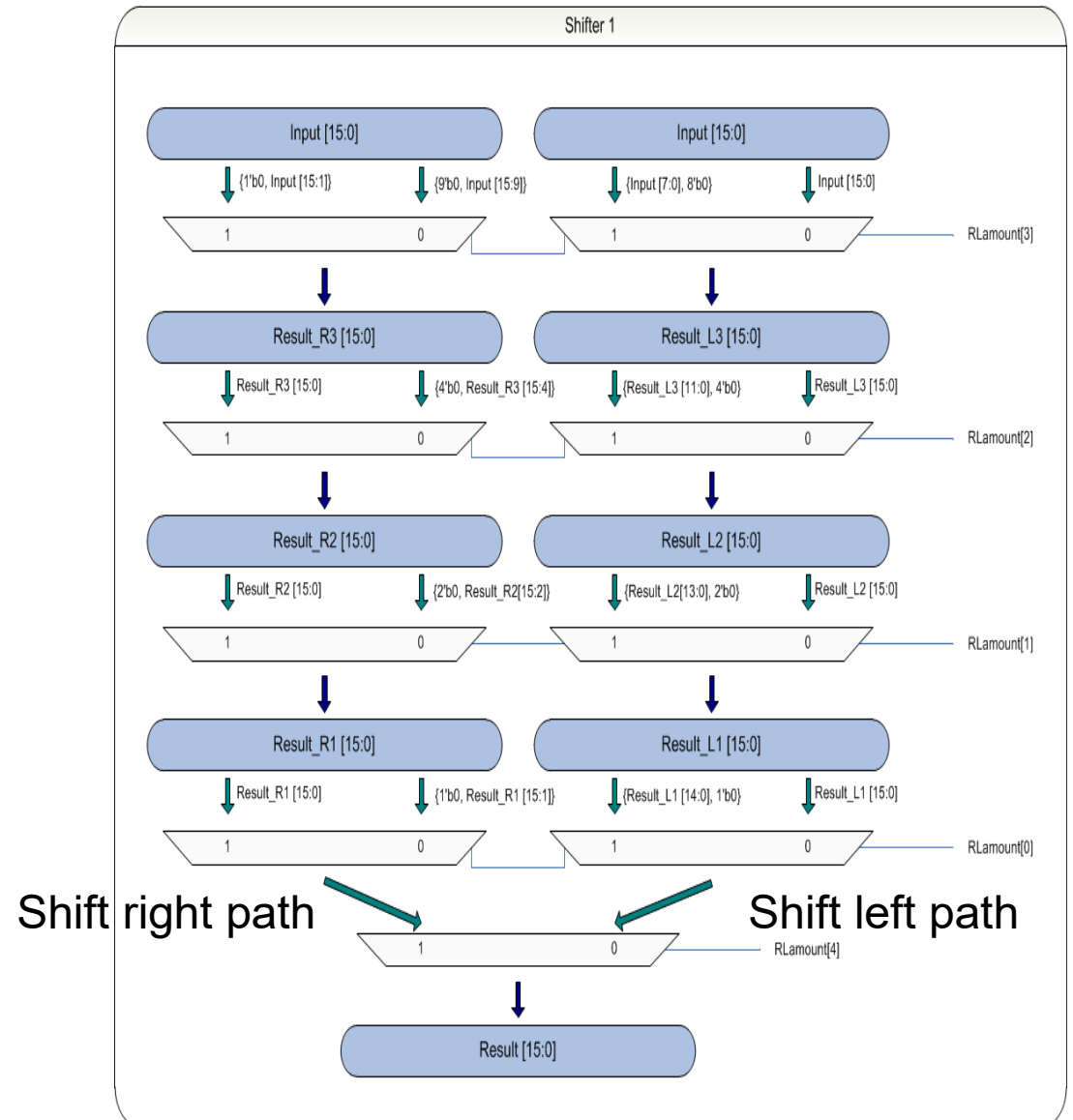
# Simple Barrel Shifter

- A 4-stage cascaded combinational logic
- Able to shift for any amounts towards bidirectionally




# TODO: Implement Shifter

- rl\_shift\_amt:
  - 2s complement signed number
  - Determines shift direction & amount
  - *If it is negative, shift right*
- lui: treat rl\_shift\_amt as ***don't care*** and simply shift left for 8 bits

```
1 module shifter
2 (
3     input [15:0] data_i,
4     input [4:0]  rl_shift_amt_i,
5     input       lui_i,
6
7     output [15:0] data_o
8 );
9
```
 
# Program Status Register (PSR)

- Output program status (e.g., overflow) based ALU's mode



# TODO: Propagate Register Inputs Properly

- Flags\_in is fed from ALU's flags\_o
- Alu\_sel is fed with ALU's selection in parallel
- PSR's flags\_o (FLCNZ) conditions
  - If alu\_sel == ADD or SUB
    - Propagate ALU's flags\_o[4] and [2] only
  - If alu\_sel == CMP
    - Propagate ALU's flags\_o[3], [1], [0]
  - Else → maintain the all registers' states

```
if clk.posedge {  
    if reset {  
        reset registers  
    } else if alu_sel = and or sub {  
        reg(F,C) = flag_i(F,C)  
    } else if alu_sel = cmp {  
        reg(L,N,G) = flag_i(L,N,Z)  
    }  
}  
flags_o = reg{F,L,C,N,Z}
```




# FLCNZ?

- Flags will be finally used by instruction decoder in the later lab
- Need to selectively propagate correct flags according to operation types
  - Signed? Unsigned?
  - [4:0] → FLCNZ in order
- Flags descriptions
  - C flag : overflow / underflow @ unsigned ADD/SUB
  - F flag : overflow / underflow @ signed ADD/ SUB
  - Z flag : A==B @ CMP
  - L flag : B<A @ unsigned CMP
  - N flag : B<A @ signed CMP
- Signed ADD/SUB or signed CMP will be inferred by instruction decoder

# Assignment



- In your report...
  - Implement and explain overflow flags in CLA16b (cla16.v) – 20%
  - Implement and explain psr input signals in ALU (alu.v) – 20%
  - Implement and explain shifter (shifter.v) – 20%
  - Implement and explain PSR (psr.v) – 20%
  - Validate waveforms in next slides (test\_alu.v, test\_shifter.v) – 20%
    - Please attach your capture of waveforms
- Use of “+/-” is NOT allowed
- Use of “^/&/|” is ALLOWED

# Desired Waveforms of test\_alu

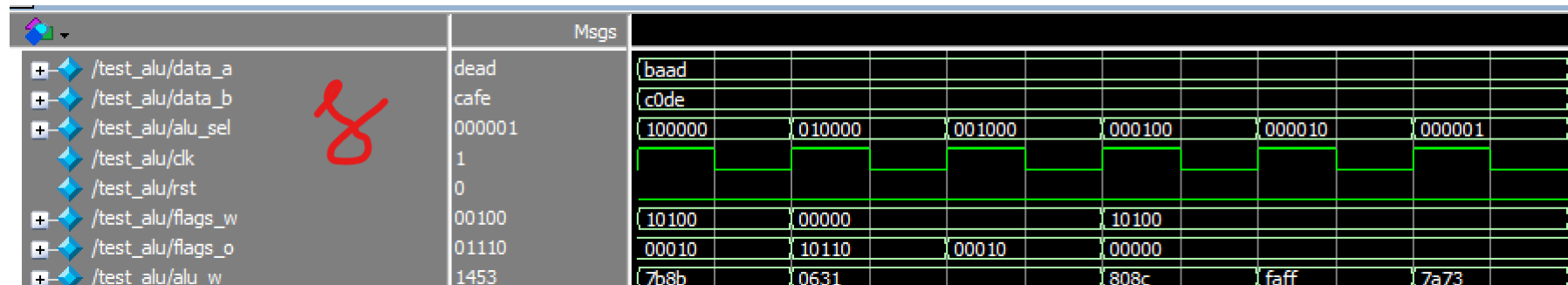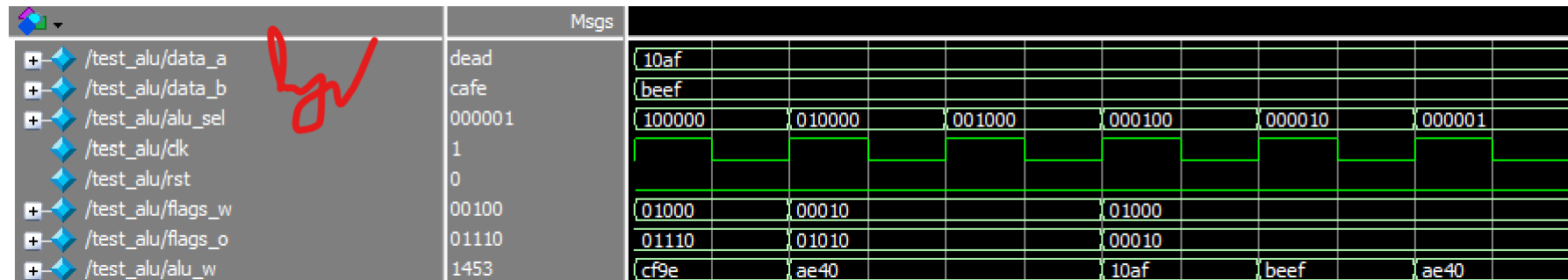 



# Desired Waveforms of test\_alu

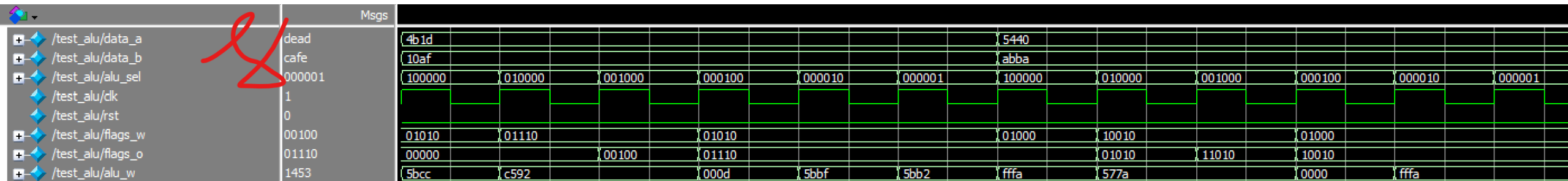 

# Waveform of test\_shifter

	Msgs																
/test_shifter/data_i	1100101011111110	1100101011111110															
/test_shifter/r1_shift_amt	0	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
/test_shifter/lui	0																
/test_shifter/data_o	cafe	cafe	95fc	2bf8	57f0	afe0	5fc0	bf80	7f00	fe00	fc00	f800	f000	e000	c000	8000	0000

		Msgs																
+ /test_shifter/data_	110010101111110	110010101111110																
+ /test_shifter/r1_shift_amt	-2	-16	-15	-14	-13	-12	-11	-10	-9	-8	-7	-6	-5	-4	-3	-2	-1	
/test_shifter/loi	0																	
+ /test_shifter/data_o	32bf	0000	0001	0003	0006	000c	0019	0032	0065	00ca	0195	032b	0657	0caf	195f	32bf	657f	fe00